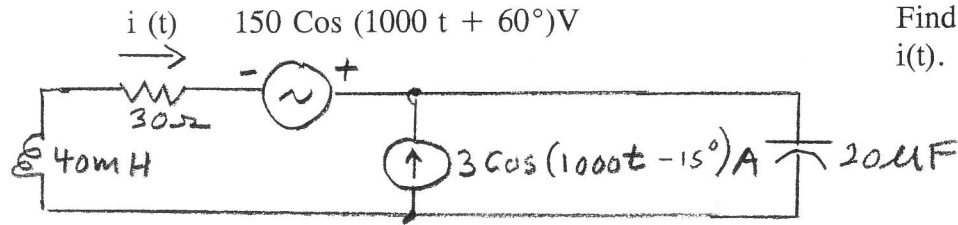


ECE 252
100 Points

Introduction to Electrical Engineering
Show your work.

Quiz 11P
Practice



Find the steady state value of $i(t)$.