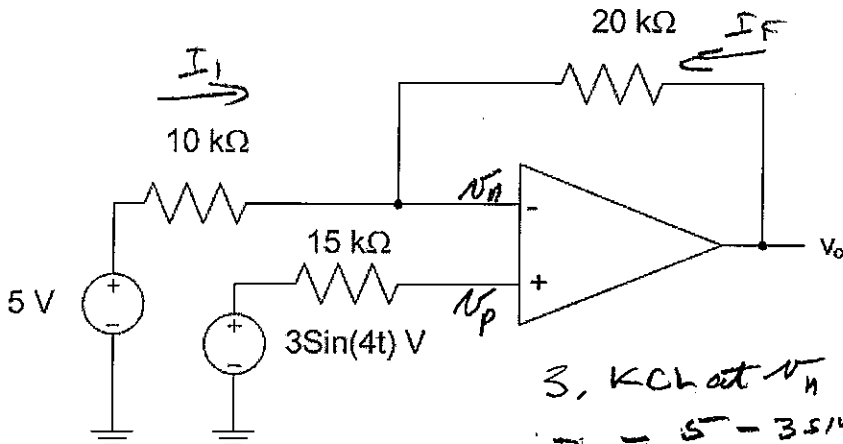


1. (50) Assume the op amp is ideal. Find  $v_o$ .



1. Find  $v_p$

$$v_p = 3 \sin 4t$$

(because there is no current in the 15 kΩ resistor)

2.  $v_n = v_p = 3 \sin 4t$

3. KCL at  $v_n$

$$I_1 = \frac{5 - 3 \sin 4t}{10k}$$

$$I_F = \frac{v_o - 3 \sin 4t}{20k}$$

$$-I_1 - I_F = 0 \rightarrow -\frac{5 - 3 \sin 4t}{10k} - \frac{v_o - 3 \sin 4t}{20k} = 0$$


$$-2(5 - 3 \sin 4t) - (v_o - 3 \sin 4t) = 0$$

$$v_o = -10 + 6 \sin 4t + 3 \sin 4t$$

$$= \underline{\underline{-10 + 9 \sin 4t \text{ V}}}$$

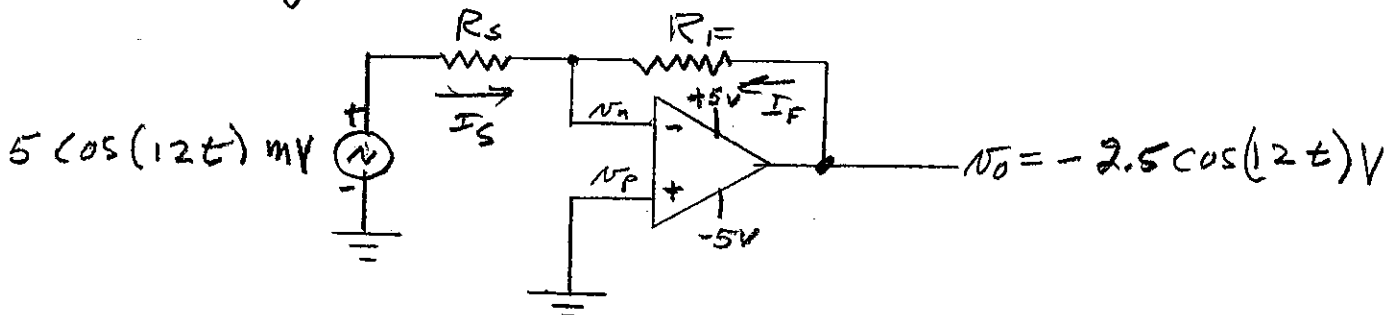2. (50) Design, sketch, and label an op-amp circuit with an input of  $5 \cos(12t)$  mV and an output of  $-2.5 \cos(12t)$  V. You have an op-amp, which may be considered ideal, and a selection of resistors from 1 kΩ to 1 MΩ. In your sketch show appropriate power supplies for the op amp. Carefully analyze the circuit to prove that it produces the desired output.

The output is negative with respect to the input, so an inverting op-amp is required.



1.  $v_p = 0$

2.  $v_n = v_p = 0$

3. Solve KCL at  $v_n$

$$I_s = \frac{5 \cos(12t) \times 10^{-3}}{R_s}$$

3. (continued)

$$I_F = \frac{-2.5 \cos(12t)}{R_F}$$

$$-I_s - I_F = 0 \rightarrow -\frac{5 \cos(12t) \times 10^{-3}}{R_s} - \frac{-2.5 \cos(12t)}{R_F} = 0$$

$$\frac{R_F}{R_s} = \frac{2.5 \cos(12t)}{5 \cos(12t) \times 10^{-3}} = 500$$

Let  $R_s = 1k\Omega$  and  $R_F = 500k\Omega$

Power supplies must span the range of the output voltage, and must be equal and opposite.