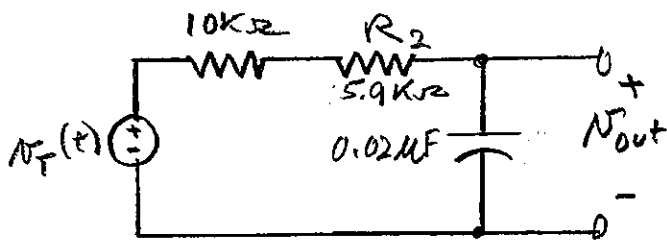


1 (70) A sensor has a Thevenin equivalent circuit which is a voltage source $v_T(t)$ in series with a $10\text{ k}\Omega$ resistor. It is to be connected to a low-pass filter so that the cutoff frequency of the entire circuit is 500 Hz . You have a $0.02\text{ }\mu\text{F}$ capacitor and an assortment of resistors. Sketch the circuit and label the components with their values. If $v_T(t)$ has a magnitude of 3 V at a frequency of 400 Hz , what is the magnitude and frequency of the output voltage of the circuit?



$$\omega_c = 2\pi f_c = 2\pi(500) = 3142 \text{ rad/s}$$

$$\omega_c = \frac{1}{RC} \rightarrow R = \frac{1}{\omega_c C}$$

$$R = \frac{1}{(3142)(0.02 \times 10^{-6})} = \underline{\underline{159\text{ k}\Omega}}$$


$$R_2 = R - 10\text{ k}\Omega = \underline{\underline{6.9\text{ k}\Omega}}$$

$$G = \frac{1}{\sqrt{1 + (f/f_c)^2}} = \frac{1}{\sqrt{1 + (400/500)^2}} = .781$$

$$G = \frac{v_{out}}{v_T} \rightarrow v_{out} = G v_T = .781(3) = \underline{\underline{2.34\text{ V}}} \text{ (magnitude of } v_{out}\text{)}$$

$$f = \underline{\underline{400\text{ Hz}}} \text{ (Frequency at input is the same as the output)}$$

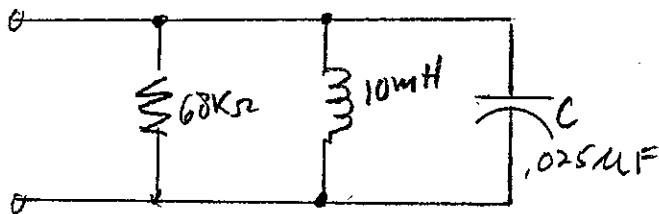2. (30) Design and sketch a parallel resonant circuit with a resonant frequency of 10 kHz and a maximum resistance of $68\text{ k}\Omega$. You have a 10 mH inductor and an assortment of capacitors and resistors.



$$\omega_0 = 2\pi f_0 = 2\pi(10\text{ k}) = 62,832 \text{ rad/s}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \rightarrow \omega_0^2 = 1/LC$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(62832)^2 (0.01)} = \underline{\underline{0.25\text{ }\mu\text{F}}}$$

R will be $68\text{ k}\Omega$ because the maximum resistance occurs at resonance and the impedance at resonance is the parallel resistance.