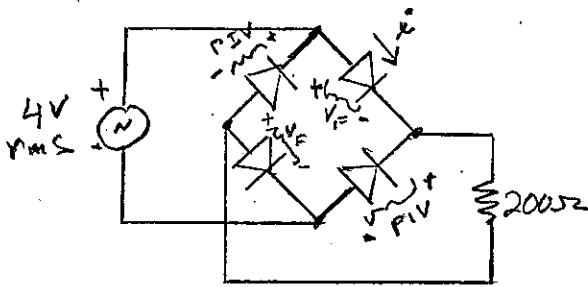


Solution

1. (35) Sketch and label the circuit for a full-wave rectifier. You have a 4 V rms, 60 Hz power supply, four silicon diodes, and a 200 Ω load. What is the maximum current in any diode? What is the minimum PIV of the diodes?



The maximum current will occur when the source voltage is highest:

$$V_{max} = 4\sqrt{2} = 5.66V$$

KVL for forward voltage:

$$-5.66 + V_F + I_{max}(200) + V_F = 0$$

$$V_F = 0.7V \text{ for silicon diodes}$$


$$I_{max} = (5.66 - 1.4) / 200 = \underline{21.31mA} \text{ (0.0213A)}$$

KVL for reverse voltage:

$$-5.66 + PIV + V_F = 0$$

$$PIV = 5.66 - 0.7 = \underline{4.96V}$$

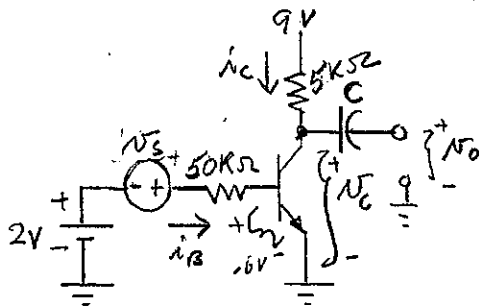2. (35) The β of the transistor below is 20. Find i_B , i_C , V_C , and V_O . Assume that the voltage drop between the base and emitter is 0.7 V.



$$KVL: -2 - V_S + i_B 50k + 0.7 = 0$$

$$i_B = \frac{1.3 + V_S}{50k}$$

$$i_C = \beta i_B = 20 \left(\frac{1.3 + V_S}{50k} \right) = \frac{1.3 + V_S}{2.5k}$$


$$KVL: 9 + 5k i_C + V_C = 0$$

$$V_C = 9 - 5k \left(\frac{1.3 + V_S}{2.5k} \right) = 9 - 2.6 - 2V_S$$

$$V_C = \underline{6.4 - 2V_S}$$

$V_O = -2V_S$ (the capacitor blocks the DC voltage)

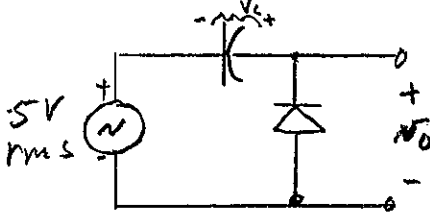3. (15) Sketch and label a clamping circuit. Describe how it works. Assume a sinusoidal source of 5 V rms and an ideal diode. Give the maximum and minimum values of the output voltage.



When the voltage source tries to make V_O negative, the diode turns on and charges the capacitor.

Eventually, the capacitor voltage (V_C) reaches $5\sqrt{2} = 7.07V$. From then on the diode remains off and $V_O = 7.07V + \text{Source voltage}$.

$$V_{O \text{ max}} = 2(7.07) = \underline{14.14V}$$

$$V_{O \text{ min}} = \underline{0}$$

4. (5) If an amplifier passes all frequencies between 10 kHz and 15 kHz, what is the approximate rise time of the amplifier?

$$t_r \approx \frac{0.35}{BW} = \frac{0.35}{15,000 - 10,000} = \underline{7\mu s}$$

5. (5) Most red LEDs have a forward voltage drop of about 2 V.