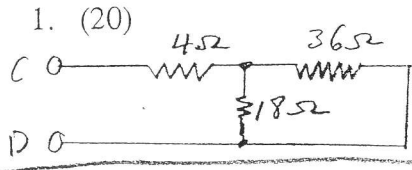


HINT: All the answers are integers.




Note || means "in parallel with"

$$R_{CD} = 16 \Omega$$

$$36 \parallel 18 = \frac{36 \cdot 18}{36 + 18} = 12$$
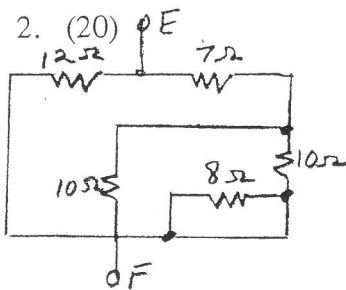
$$R_{CD} = 4 + 12 = \underline{16 \Omega}$$




8Ω is "shorted out!"

$$10 \parallel 10 = 5 \Omega$$

$$7 + 5 = 12$$

$$R_{EF} = \frac{12 \cdot 12}{12 + 12} = 6 \Omega$$

$$R_{EF} = \underline{6 \Omega}$$

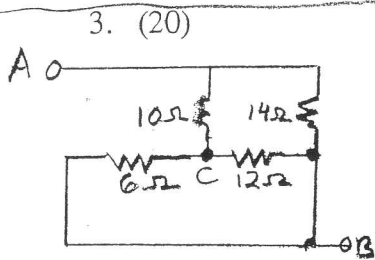


$$12 \parallel 6 = 4 \Omega$$

$$10 + 4 = 14$$

$$R_{AB} = \frac{14 \cdot 14}{14 + 14} = 7 \Omega$$

$$R_{AD} = \underline{7 \Omega}$$

4. (20)

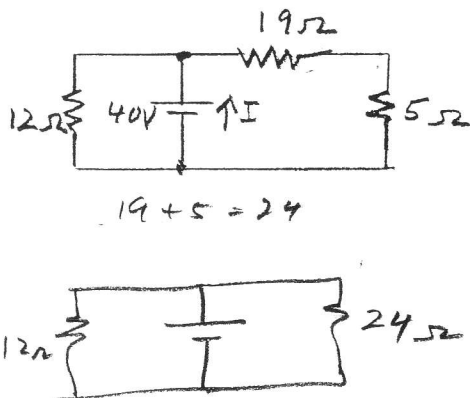


Use network reduction (combining resistors in series and parallel) to find I.

$$24 \parallel 12 = \frac{24 \cdot 12}{24 + 12} = 8 \Omega$$

$$I = \frac{V}{R} = \frac{40}{8} = \underline{5A}$$

5. (20)

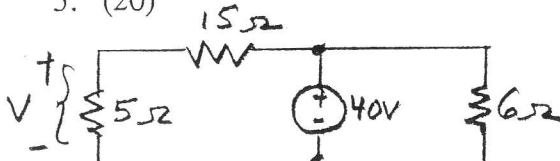

Use the voltage divider formula to find V.

$$V_2 = \frac{V_s R_2}{R_1 + R_2} = \frac{40(5)}{15 + 5} = \underline{10V}$$