
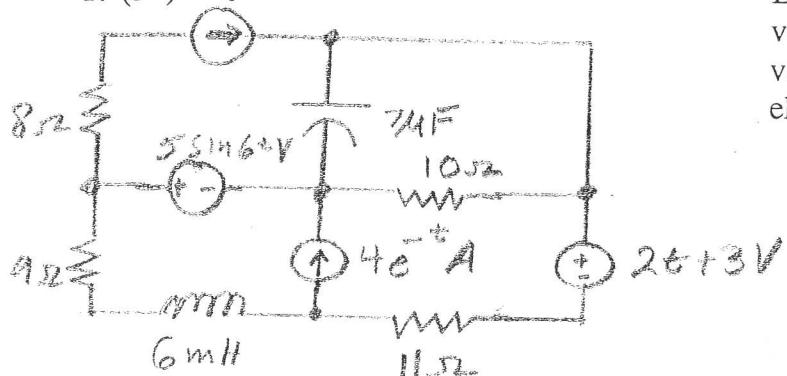


1. (50) $i_2 = 12 \text{ A}$

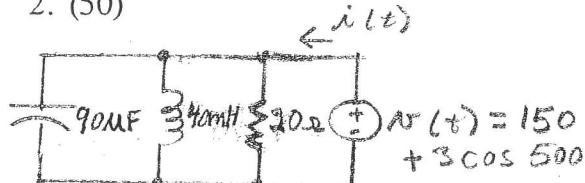

Label the diagram with currents and voltages. Write equations to solve for the voltage across and the current through each element. Do not solve.

2. (50)



Find $i(t)$. At $t=0$, the current in the inductor is 8A downward.

Simplify your answer.