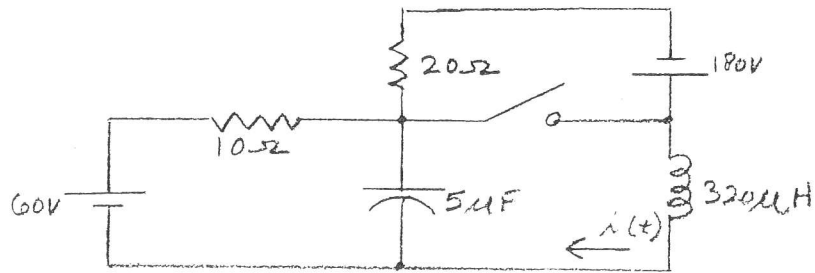


ECE 252
100 Points

Introduction to Electrical Engineering
Show your work.

Quiz 9P
Practice



Find $i(t)$ for $t \geq 0+$. The switch is closed at $t = 0$.