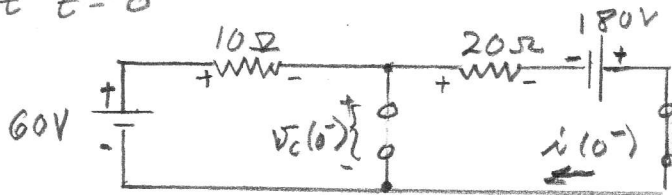


at $t = 0^-$



$$\text{KVL: } -60 + 10i(0^-) + 20i(0^-) - 180 = 0$$


$$30i(0^-) = 240$$

$$i(0^-) = 240/30 = \underline{8A}$$

$$\text{KVL: } -60 + 10(8) + v_c(0^-) = 0$$

$$v_c(0^-) = 60 - 80 = \underline{-20V}$$

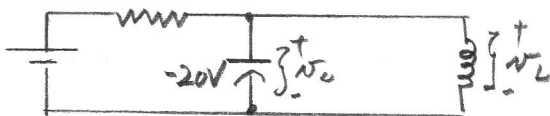at $t = 0^+$ $i(0^+) = i(0^-) = \underline{8A}$
 $v_c(0^+) = v_c(0^-) = \underline{-20V}$



$$\text{KVL: } v_L(0^+) - v_c(0^+) = 0$$


$$v_L(0^+) = v_c(0^+) = -20$$

$$v_L = L \frac{di}{dt}$$

$$i'(0) = v_L / L = -20 / 320 \times 10^{-6}$$


$$i'(0) = \underline{-62,500 A/s}$$

Source Transformation 104

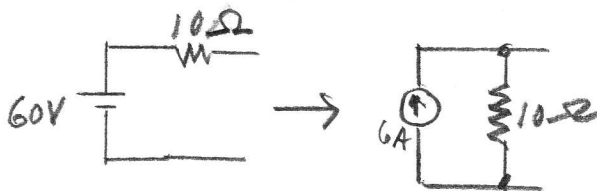

Find $i(t)$ for $t \geq 0^+$. The switch is closed at $t = 0$.

at $t = \infty$:

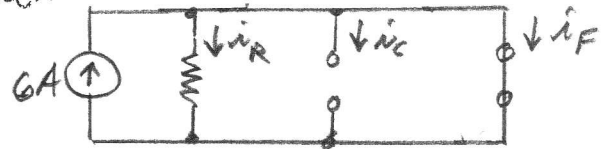


$$i_R = V/R = 0, \quad i_L = 0$$

$$\text{KCL: } -6 + i_R + i_L + i_F = 0$$

$$i_F = \underline{6A}$$

General circuit for $t > 0$

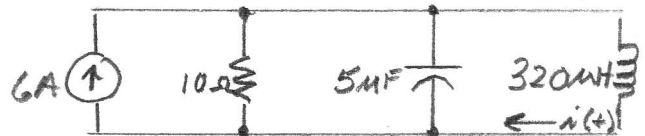

$$\alpha = \frac{1}{2RC} = \frac{1}{2(10)(5 \times 10^{-6})} = \underline{10,000 \text{ rad/s}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(320 \times 10^{-6})(5 \times 10^{-6})}}$$

$$= \underline{25,000 \text{ rad/s}}$$

$\omega_0 > \alpha$, \therefore underdamped

$$i(t) = i_F + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$i(0) = 8 = 6 + B_1 \rightarrow B_1 = 2$$

$$i'(t) = -\alpha B_1 e^{-\alpha t} \cos \omega_d t - \omega_d B_1 e^{-\alpha t} \sin \omega_d t$$

$$- \alpha B_2 e^{-\alpha t} \sin \omega_d t + \omega_d B_2 e^{-\alpha t} \cos \omega_d t$$

$$i'(0) = -62,500 = -\alpha B_1 + \omega_d B_2$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \underline{22,913 \text{ rad/s}}$$

$$-62,500 = -(10,000)(2) + (22,913)(B_2)$$

$$B_2 = (20,000 - 62,500) / 22,913 = \underline{-1.85}$$

$$i(t) = 6 + 2 e^{-10000t} \cos 22913t$$

$$- 1.85 e^{-10000t} \sin 22913t \text{ A}$$